
2015

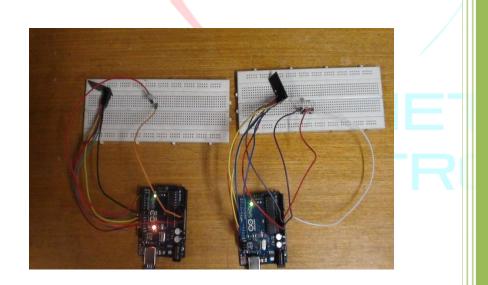

Interfacing NRF24L01 Transceiver with Arduino UNO



Author: Vivek g s

Transmitting data through wireless can be done by various hardware modules like XBEE, HC-05 Bluetooth module, RF ASK module etc. These modules operate on different frequency band and they are very much costlier, if you are looking out for a wireless transceiver device which uses ultralow power and with less cost and it can also transmit and receive data up to 1Km range NRF24L01 is the device.


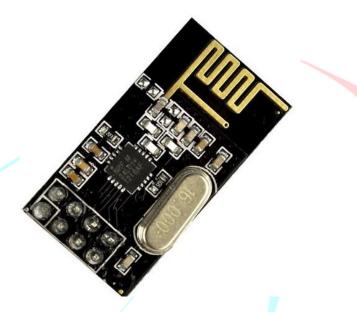


Figure 1 - nRF24L01 module

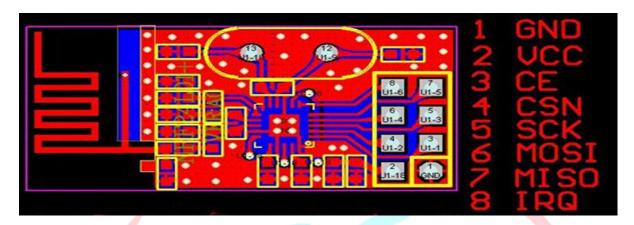The nRF24L01+ is a single chip 2.4GHz transceiver with an Enhanced shock burst protocol embedded in it, which operates on a very low power (i.e. 3.3V). In this application note we are interfacing nRF24L01+ module with <u>Arduino UNO</u> to turn ON an LED, whenever the LDR value reaches certain limit on the transmitter end a LED on the receiver side will glow.



PIN Configuration:



 $Figure\ 2-nRF24L01\ pin\ outs$

Pin Description:

GND	Connects to System Ground
IRQ	Maskable interrupt pin. Active Low
MISO	SPI Slave Data Output
MOSI	SPI Slave Data Input
SCK	SPI Slave Data Input
CSN	SPI Chip Select
CE	Chip Enable Activates RX or TX mode. CE
	= 0 makes the chip to go into Stand-by
VCC	Connects to Power Supply (3.3V).

Pin connections:


Arduino UNO	nRF24L01
GND	GND
3.3V	VCC
Pin-9	CE
Pin-10	CSN
Pin-13	SCK
Pin-11	MOSI
Pin-12	MISO
No connection	IRQ

 ${\it \# 9/3, 2nd floor, Sree Laksmi \ Complex, opp, to \ Vivekananda \ Park, Girinagar, Bangalore - 560085,}$

 ${\bf Email: info@tenettech.com, Phone: 080-26722726}$

Interfacing nRF24L01+ module with Arduino UNO

Transmitter Block diagram

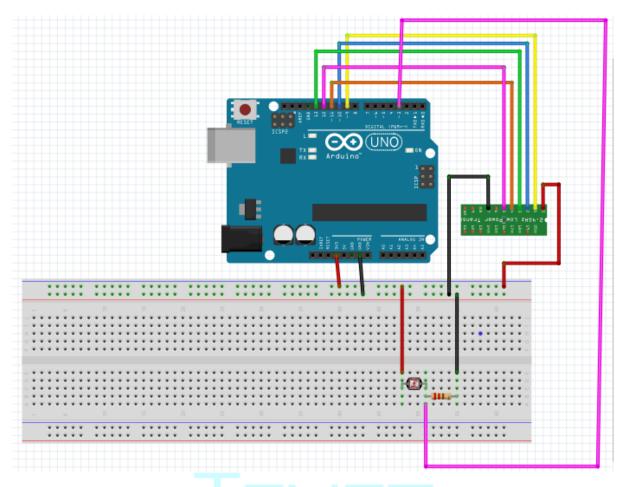

 $Figure \ 3-Transmitter \ circuit \ diagram$

TECHNETRONICS

 ${\it \# 9/3, 2nd floor, Sree Laksmi \ Complex, opp, to \ Vivekananda \ Park, Girinagar, Bangalore - 560085,}$

Receiver:

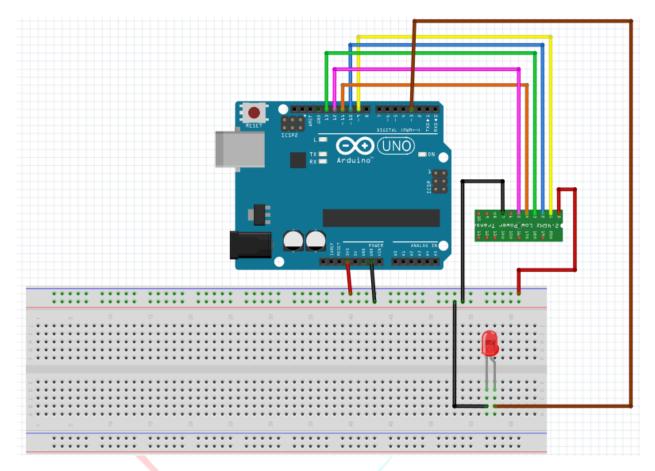


Figure 3 – Receiver circuit diagram

Code:

Transmitter:

#include <SPI.h>

#include "nRF24L01.h"

#include "RF24.h"

RF24 radio(9,10);

 ${\it \# 9/3, 2} nd \ floor, Sree Laksmi \ Complex, opp, to \ Vivekan and a \ Park, Girinagar, Bangalore - 560085,$

```
const uint64_t pipe = 0xE8E8F0F0E1LL;
int SW1 = A0;
int value[2];
void setup(void){
Serial.begin(9600);
radio.begin();
radio.openWritingPipe(pipe);}
void loop(void)
value[0] = analogRead(SW1);
radio.write( value, sizeof(value) );
}
Receiver:
#include <SPI.h>
#include "nRF24L01.h"
#include "RF24.h"
int value[2];
RF24 radio(9,10);
const uint64_t pipe = 0xE8E8F0F0E1LL;
int LED1 = 2;
void setup(void){
\# 9/3, 2nd floor, SreeLaksmi Complex, opp, to Vivekananda Park, Girinagar, Bangalore - 560085,
Email: info@tenettech.com, Phone: 080 - 26722726
```

```
Serial.begin(9600);
radio.begin();
radio.openReadingPipe(1,pipe);
radio.startListening();
pinMode(LED1, OUTPUT);}
void loop(void){
if (radio.available()){
 bool done = false;
 while (!done){
   done = radio.read(value, sizeof(value));
   Serial.println(value[0]);
   if(value[0]>900){
digitalWrite(LED1, HIGH);
 else{
  digitalWrite(LED1, LOW);}}}
Libraries to be included:
https://github.com/maniacbug/RF24
\# 9/3, 2nd floor, SreeLaksmi Complex, opp, to Vivekananda Park, Girinagar, Bangalore - 560085,
Email: info@tenettech.com, Phone: 080 - 26722726
```

Result:

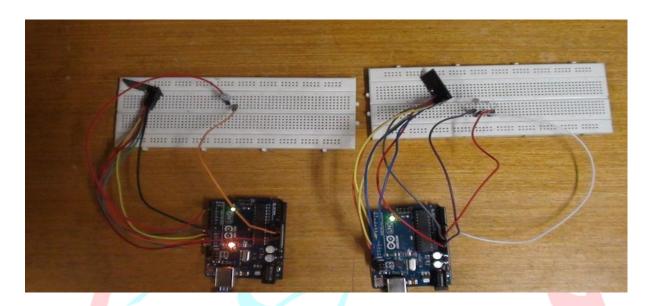


Figure 3 – Without any light

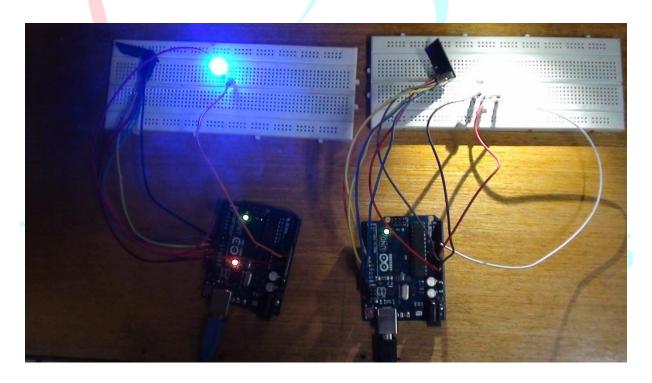


Figure 4 – Output

 ${\it \# 9/3, 2} nd \ floor, Sree Laksmi \ Complex, opp, to \ Vivekan and a \ Park, Girinagar, Bangalore - 560085,$

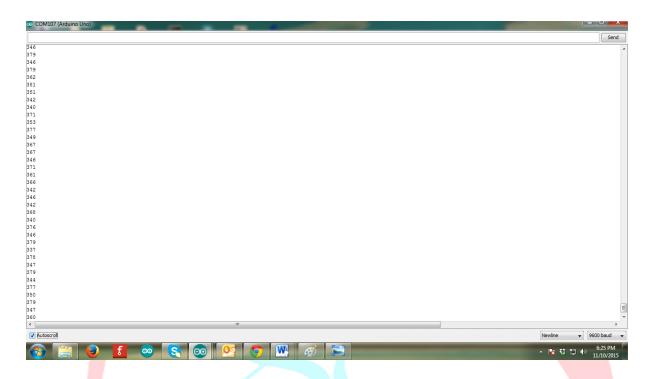


Figure 5 – Analog readings of LDR on serial monitor

For product information:

- 1. http://www.tenettech.com/product/5294/nrf24l01module
- 2. HTTP://WWW.TENETTECH.COM/PRODUCT/202/ARDUINO-UNO-ARDUINO-UNO-R3
- 3. HTTP://WWW.TENETTECH.COM/PRODUCT/2609/BASIC-BREADBOARD

TECHNETRONICS

For more information please visit: www.tenettech.com

For technical query please send an e-mail: info@tenettech.com

9/3, 2nd floor, SreeLaksmi Complex, opp, to Vivekananda Park, Girinagar, Bangalore - 560085,